

Present state	Next state				Output $s$			
	$ab = 00$	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

**Figure 6.41** State table for the serial adder FSM.