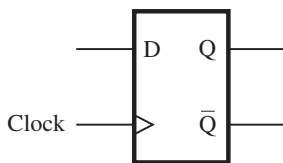


(a) Circuit



(b) Graphical symbol

**Figure 7.11** A positive-edge-triggered D flip-flop.