 


(a) Circuit



(b) Timing diagram

Figure 7.12 Comparison of level-sensitive and edge-triggered D storage elements.