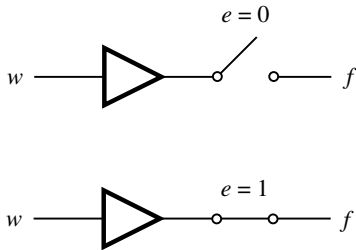


(a) Symbol



(b) Equivalent circuit

e	w	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table

Figure 7.1 Tri-state driver.