
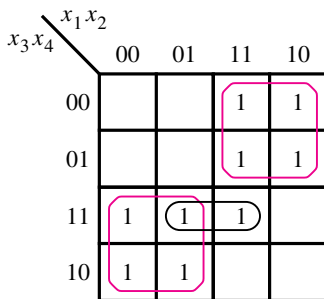


(a) Function  $f_1$

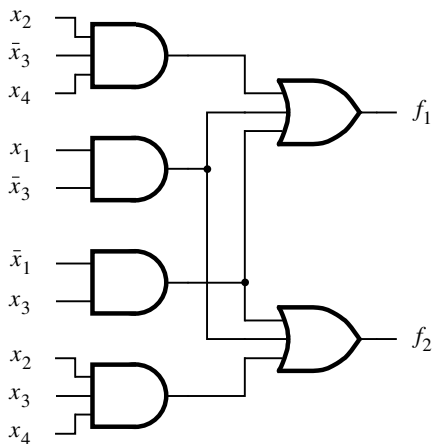

(b) Function  $f_2$



(c) Combined circuit for  $f_1$  and  $f_2$

**Figure 2.64** An example of multiple-output synthesis.