

Present state	Next state	Output z
	$w = 0$ $w = 1$	$w = 0$ $w = 1$
A	A B	0 0
B	A B	0 1

Figure 6.24 State table for the FSM in Figure 6.23.