

A
B

Present state	Next state		Output	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
y	Y	Y	z	z
0	0	1	0	0
1	0	1	0	1

Figure 6.25 State-assigned table for the FSM in Figure 6.24.