

**Figure 3.6** Circuit that multiplies an eight-bit unsigned number by 3.