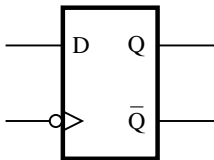


(b) Timing diagram



(c) Graphical symbol

Figure 5.9 Master-slave D flip-flop.