



Figure 2.28 Using NOR gates to implement a product-of-sums.