



Figure 6.5 A general sequential circuit with input w , output z , and two state flip-flops.