 


(a) Block diagram



(b) Detailed diagram

Figure 3.4 A decomposed implementation of the full-adder circuit.