(a) Canonical sum-of-products
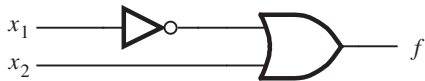

(b) Minimal-cost realization

Figure 2.20   Two implementations of the function in Figure 2.19.